



# WPI

---

# IMGD 3100 – Novel Interfaces for Interactive Environments: Electricity

Robert W. Lindeman

Associate Professor

Interactive Media & Game Development

Human Interaction in Virtual Environments (HIVE) Lab

Department of Computer Science

Worcester Polytechnic Institute

[gogo@wpi.edu](mailto:gogo@wpi.edu)

---

## Overview


---

- ❑ So you've built some circuits, made some stuff blink, read values from devices, etc.
- ❑ Do you understand a little better what's going on with all this ECE stuff?
- ❑ Since almost none of you have any ECE background, how can I expect you to do this stuff?!?!??!
- ❑ Let's see what we know...
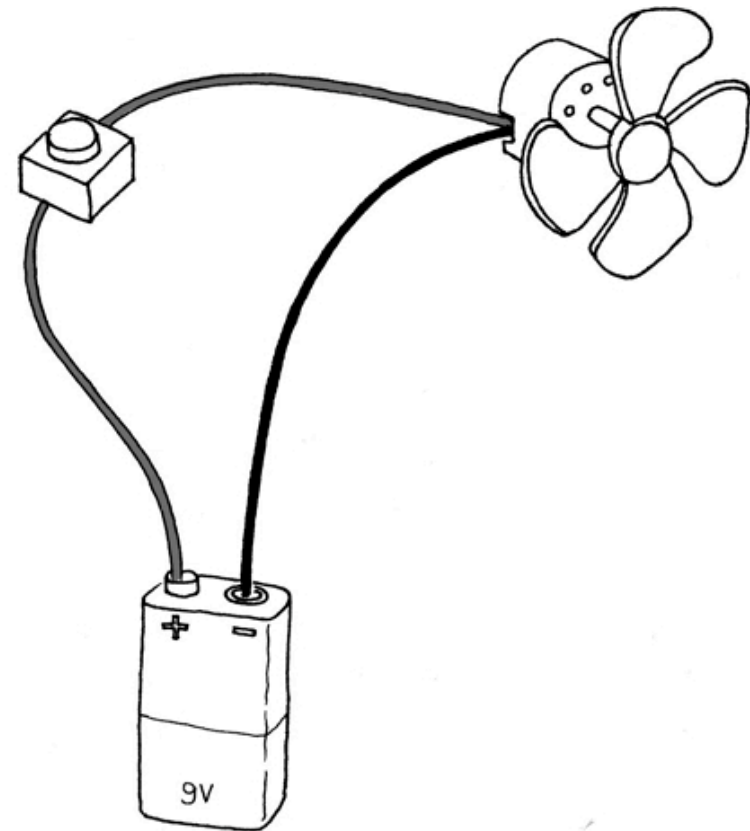
## Simple Current Flow

---


- Parts of the system
  - Power source
  - Output device
    - Motor
  - Switch
  - Conduits
- What if you switch the ***polarity?***


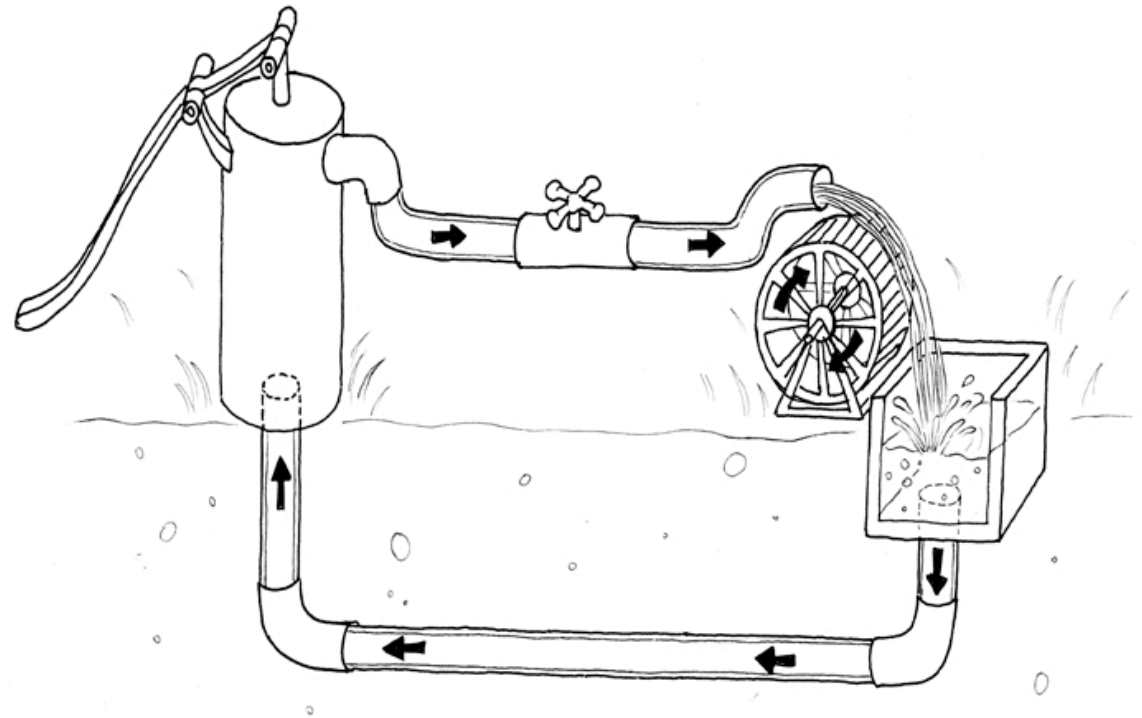
# Water Analogy

---


- Water source and pump
  - Battery
- Tap
  - Switch
- Water wheel
  - Motor
- Open tap, water drives the wheel


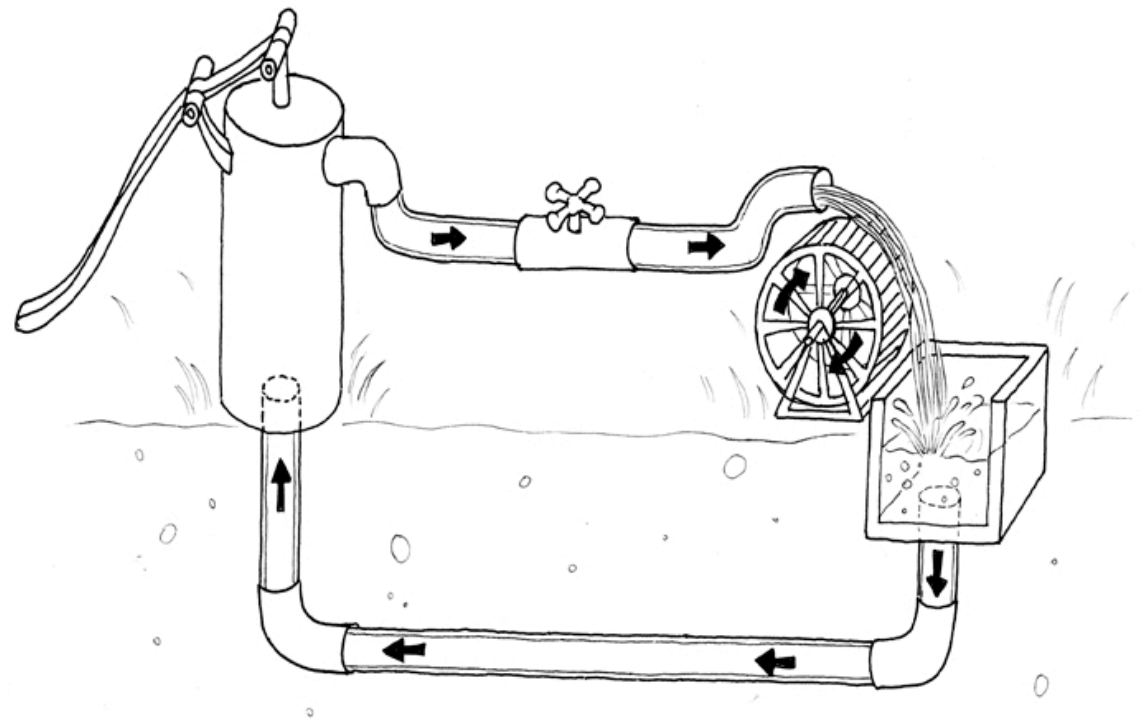
# Water Analogy: Important Points


---

- Two factors
  - Water Pressure
  - Flow rate
- Governed by
  - the power of the pump
  - Size of the pipe/  
friction of wheel
- Larger pipe +  
stronger pressure  
= faster spin


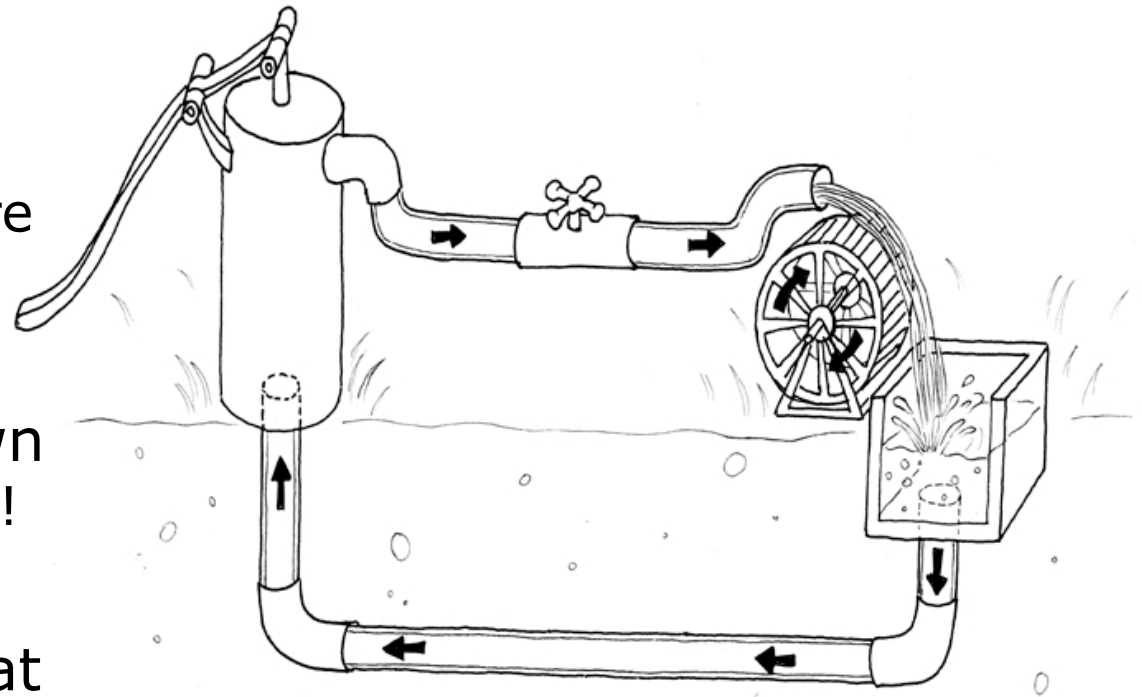
# Water Analogy: More Detail

- Larger pipes = less resistance
  - After some point, need more pressure to fill the pipe
- At some point, the wheel will breakdown
  - too much pressure!
- Some of the energy will come out as heat (from the wheel axel) or something else
  - Same in ECE



## Making the Connection to ECE

---

- Pressure is produced by the pump
- Resistance produced by pipes
- Resistance produced by wheel
- The flow rate (e.g., liters/second)
- In ECE:
  - Power source (battery, wall wart) is the pump
  - Wires, resistors, etc. are the pipes
  - Devices are the wheel
  - Current is the flow rate

## Arduino Programming

---

- We know that  
**digitalWrite( 13, HIGH );**  
will turn on the LED attached to pin 13
- But what does this *mean*?
- It means the pin will be driven with 5 volts.
  - What is a *Volt*?



## Voltage

---

- Voltage is related to potential energy
- Recall:
  - if you lift something off the ground, it gains potential energy
  - If you let go, it releases the potential energy stored when you lifted it.
- Assume you have a positive charge and a negative charge
- They are attracted to each other, and if you pull them apart, your effort is stored as potential energy

## Voltage (cont.)

---

- If you release them, the charges jump back together (like the weight)
- For the weight, potential energy is calculated by plugging the height into:  
$$E = mgh$$
 (mass x gravity x height)
- For charges, height is analogous to voltage
- For the potential energy, you multiply the voltage times the charge you are raising
  - The “electronic height” of a charge

## Voltage (cont.)

---

- So, what if, while the weight is being held up, someone puts a table underneath it?
  - Does the potential change?
  - How do you explain this?
  
- Potential is always measured between two points
  - It is an ***across*** variable.
  
- Same for voltage
  - Ground is one of the points by default



# Current

---

- So, circuits provide paths for charges that have been raised to some potential to flow back down to ground
- This *flow of charge* is called Current
- Current is a ***through*** variable
- It is the first derivative of charge
  - The number of Coulombs of charge that pass a point per second
  - A *Coulomb* is about  $6 \times 10^{18}$  electrons
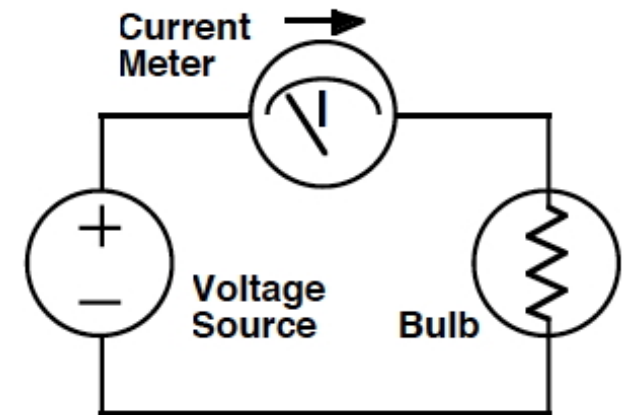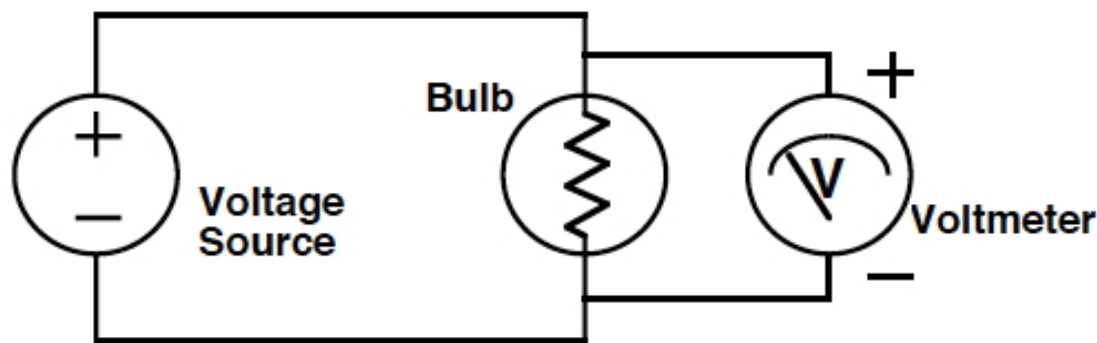
## Voltage & Current

- Voltage is measured using a voltmeter
- Current is measured using a current meter (a.k.a. an *ammeter*)



- Direction (polarity) is important too!

## Voltage & Current (cont.)

---

- Kirchhoff's Voltage Law (KVL)
  - The voltage that you drop on one side of a circuit must be equal to the amount of voltage you raised on the other side.
  - You can only fall the height you were raised
  
- Kirchhoff's Current Law (KCL)
  - Current is a conserved quantity
  - If some amount of current flows into a part of a circuit, the exact same amount must flow out.

## Making the Connection to ECE

---

- A 9V battery is a pump (9V of pressure)
  - Unit is **Volts (V)** named after the inventor of the battery
- Flow rate is called **current**, and is measured in amperes or **Amps (A)**
  - After André-Marie Ampère
- Higher voltage (pressure) lets you spin the wheel faster
- Higher flow rate (current) lets you spin a larger wheel

# Making the Connection to ECE

---

- Resistance opposing the flow of current over any path is called **resistance**, and is measured in **Ohms ( $\Omega$ )**
  - After German physicist Georg Ohm
- This guy also gave us an important law
  - **Ohm's Law** describes the relationship between current, voltage, and resistance.
  - The **resistance** in a circuit will determine the amount of **current** that will flow through it, given a certain **voltage** supply.



# Ohm's Law

---

- If we measure the current from a 9V battery plugged into a simple circuit, the current will drop if we add more resistance.
- Formally stated:  
$$R \text{ (resistance)} = V \text{ (voltage)} / I \text{ (current)}$$
$$V = R * I$$
$$I = V / R$$
- Why “I” for current?

## Watts (W)

---

- Rate of energy conversion
  - Work is done at a rate of one watt when one ampere flows through a potential difference of one volt
- $$1W = 1V * 1A$$
- A 100 W bulb burning for 1 hour would consume 100 watt-hours (W-h)
  - A 40 W bulb could burn for 2.5 hours and consume the same energy (100 W-h)

## More Terms

---

- Capacitance
  - The ability for a body to hold a charge
  - Used for
    - Temporary power storage (UPS, laptops)
    - Smoothing a power signal
- Transistor
  - Solid-state electronic switch
- MOSFET
  - Metal–Oxide–Semiconductor Field-Effect Transistor
  - When a Voltage is present on a specific pin, current flows between the other two pins
  - Used to amplify or switch electronic signals
- Relay
  - Electrically operated switch
  - Current creates a magnetic field which "throws" the switch


## Varying the Output

---

- We've seen how easy it is to turn things ON and OFF
  - But this quickly becomes too limiting!
- Given Ohm's Law, how can we change the brightness of an LED?
  - Increase the resistance
    - Maybe with a resistor ladder
- How else?
  - Quickly blink it ON and OFF
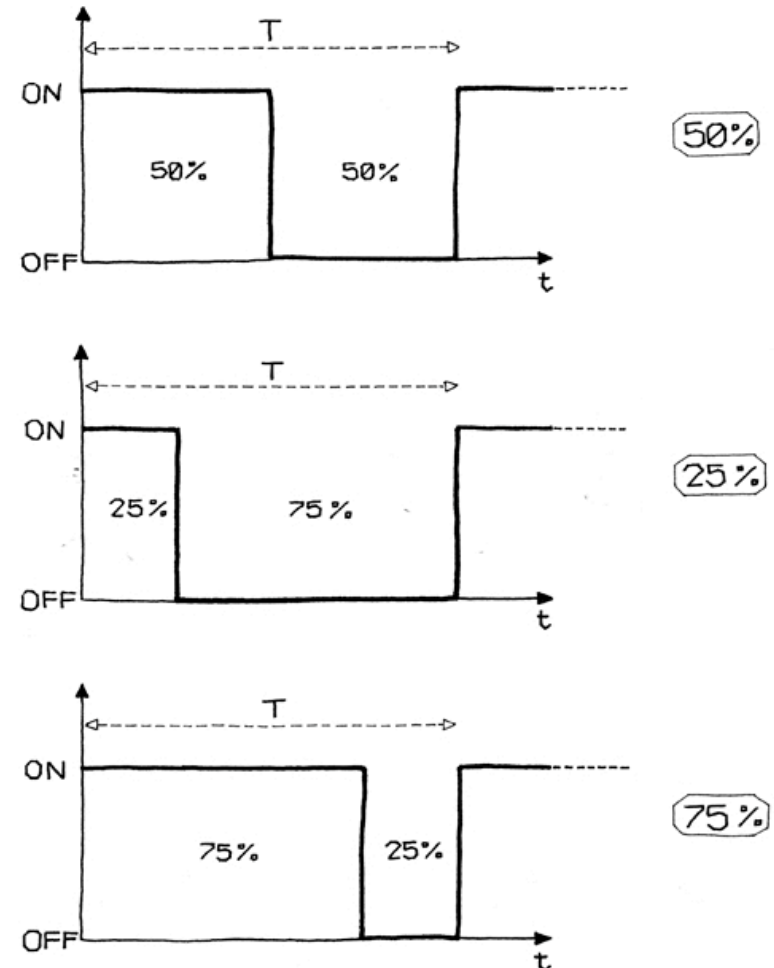
## Pulse-Width Modulation (PWM)

- Vary the percentage of time over a given period that an output is HIGH (or LOW)
  - This is how traditional dimmer switches work
- Period
  - Total time for the signal
- Duty Cycle
  - Percentage of the period the signal is HIGH



## Persistence of Vision

---

- Human eye won't notice down to a certain point
  - <http://hackedgadgets.com/2008/11/05/arduino-rotating-led-display/>

## Further Reading

---

- [http://antonine-education.co.uk/electronics\\_as.htm](http://antonine-education.co.uk/electronics_as.htm)